
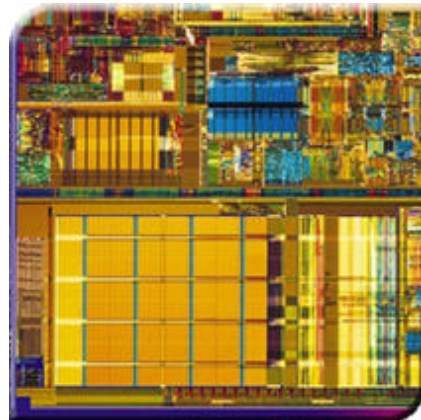


# Computer Architecture

## Lecture 6 Multi-Cycle Datapath

---

 


Prof. Jongmyon Kim


 
# Review: Single Cycle Implementation

- Calculate cycle time assuming negligible delays except:
  - memory (2ns), ALU and adders (2ns), register file access (1ns)




# Summary (cont.)

| Instruction Class | Instruction Fetch | Register Read | ALU Operation | Data Access | Register Write | Total Time |
|-------------------|-------------------|---------------|---------------|-------------|----------------|------------|
| Load word         | 2ns               | 1ns           | 2ns           | 2ns         | 1ns            | 8ns        |
| Store word        | 2ns               | 1ns           | 2ns           | 2ns         |                | 7ns        |
| R-format          | 2ns               | 1ns           | 2ns           |             | 1ns            | 6ns        |
| Branch            | 2ns               | 1ns           | 2ns           |             |                | 5ns        |

- Single cycle datapath
  - Design for the worst case
  - Need to make the cycle time = 8ns per cycle
- Multi-cycle datapath
  - Design for each individual instruction class
  - For the above example: cycle time = 2ns
  - Lw=10ns (5 cycles), sw=8ns (4 cycles), R-format=8ns(4 cycles), beq=6ns (3 cycles)
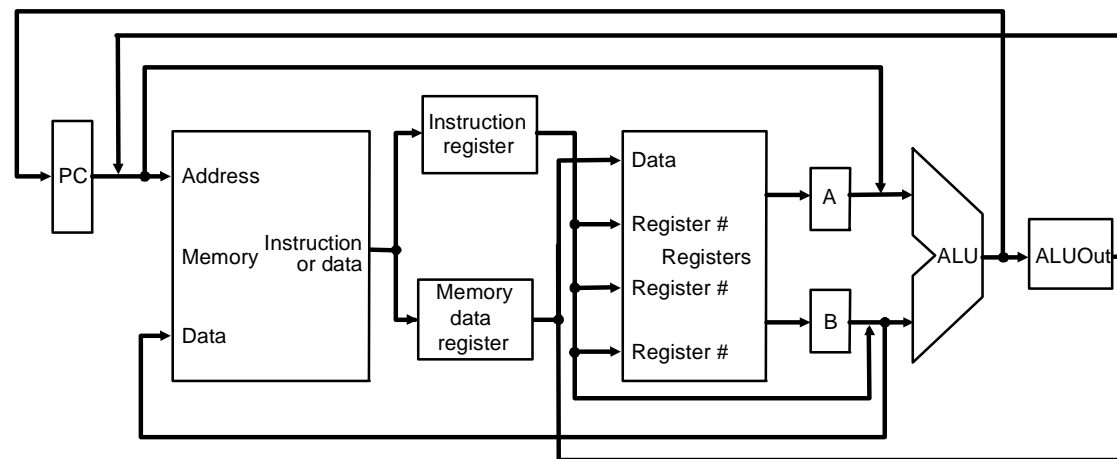
# Where we are headed

- Single Cycle Problems:
  - what if we had a more complicated instruction like floating point?
  - wasteful of area
- One Solution:
  - use a “smaller” cycle time
  - have different instructions take different numbers of cycles
  - a “multicycle” datapath:



# Multi-cycle Approach

---

## □ Single-cycle design

- Clock period is limited by the “worst case instruction timing” (which instructions?)
- Violate Amdahl’s Law: Make the common case faster
- Require duplication of some functional units such as adders for PC generation and an ALU for arithmetic

## □ Multi-cycle design

## □ We will be reusing functional units and memory

- ALU used to compute address and to increment PC
- Memory used for instruction and data

## □ Our control signals will not be determined solely by instruction


- e.g., what should the ALU do for a “subtract” instruction?

## □ We’ll use a finite state machine for control

- State elements needed for transient data produced by “the same instruction”


# Simple Implementation
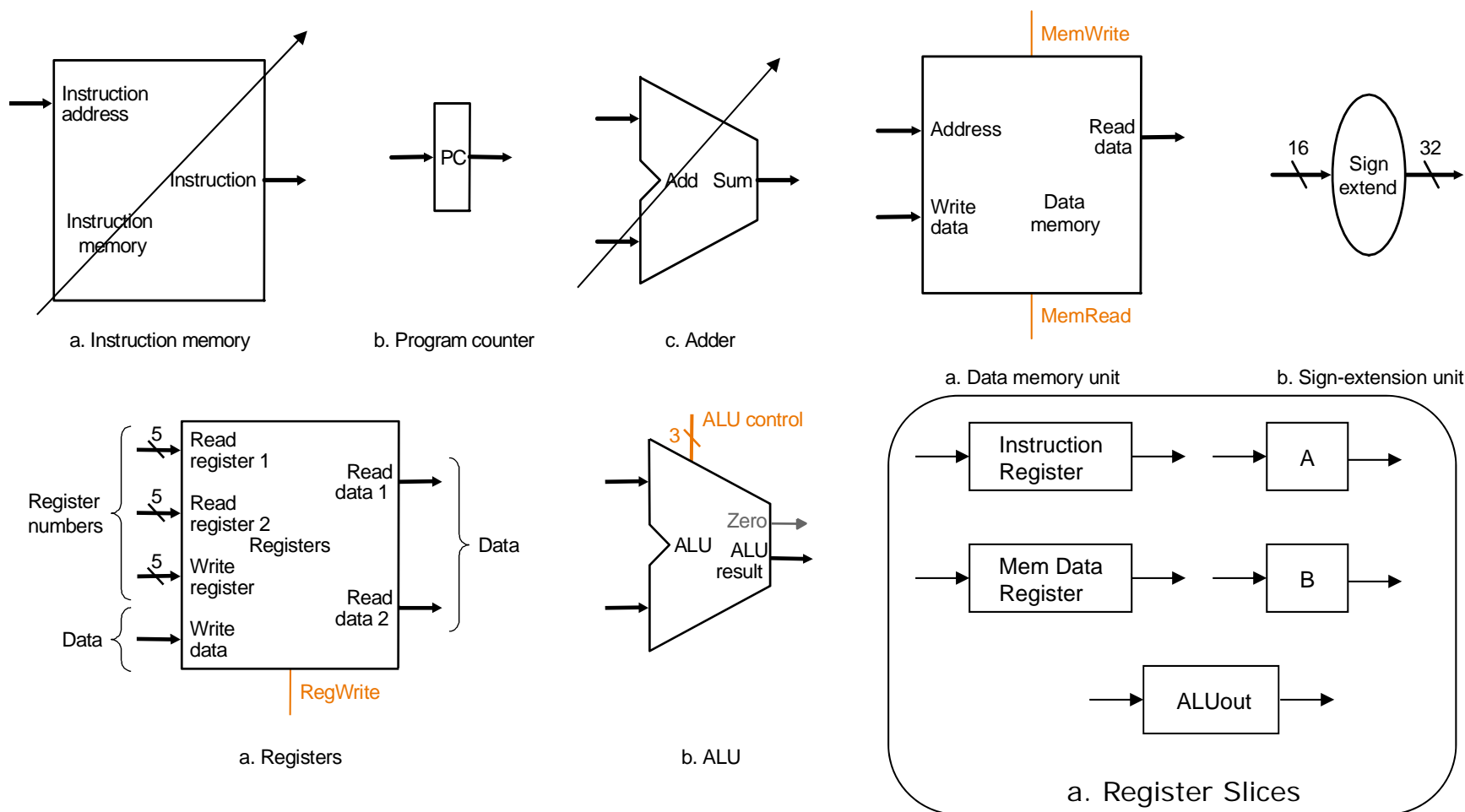
## □ Single-Cycle Datapath vs. Multi-Cycle Datapath




# Single-Cycle vs. Multi-Cycle Datapath

## Single-Cycle Datapath

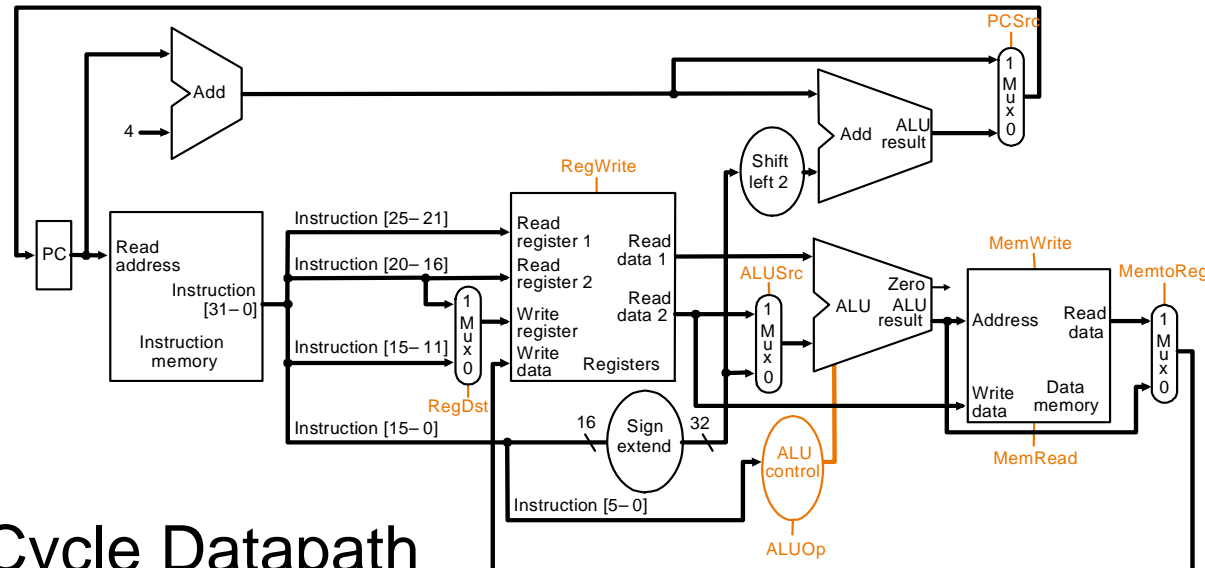


## Multi-Cycle Datapath

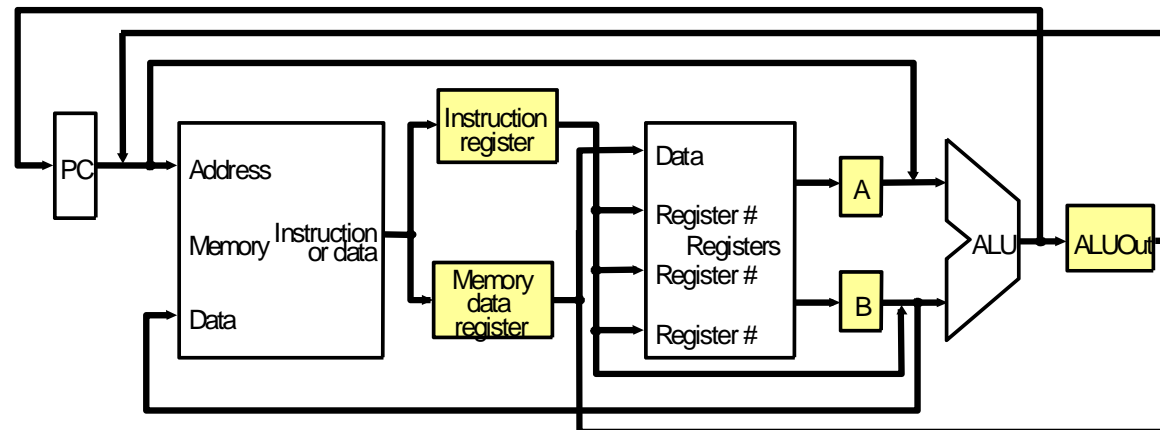

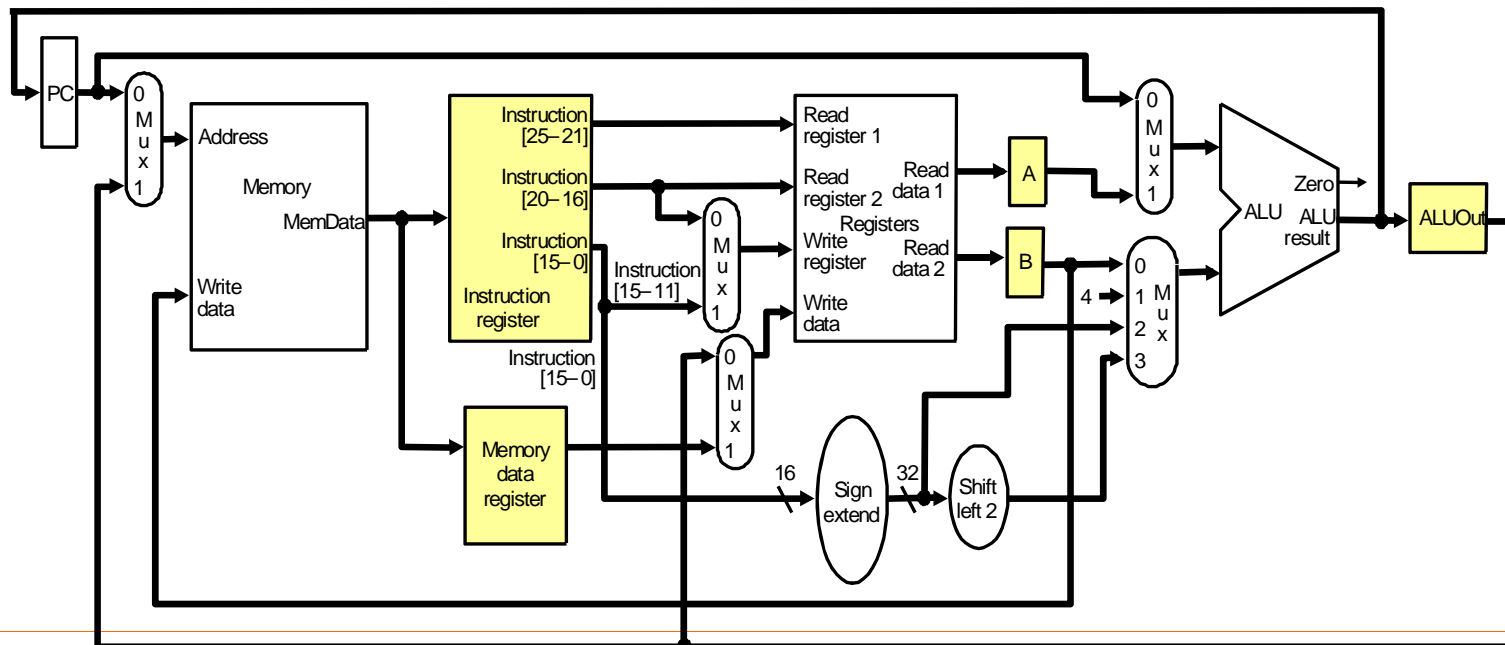
# Multi-Cycle Approach

- Break up the instructions into steps, each step takes a cycle
  - balance the amount of work to be done
  - restrict each cycle to use only one major functional unit
- At the end of a cycle
  - store values for use in later cycles (easiest thing to do)
  - introduce additional “internal” registers





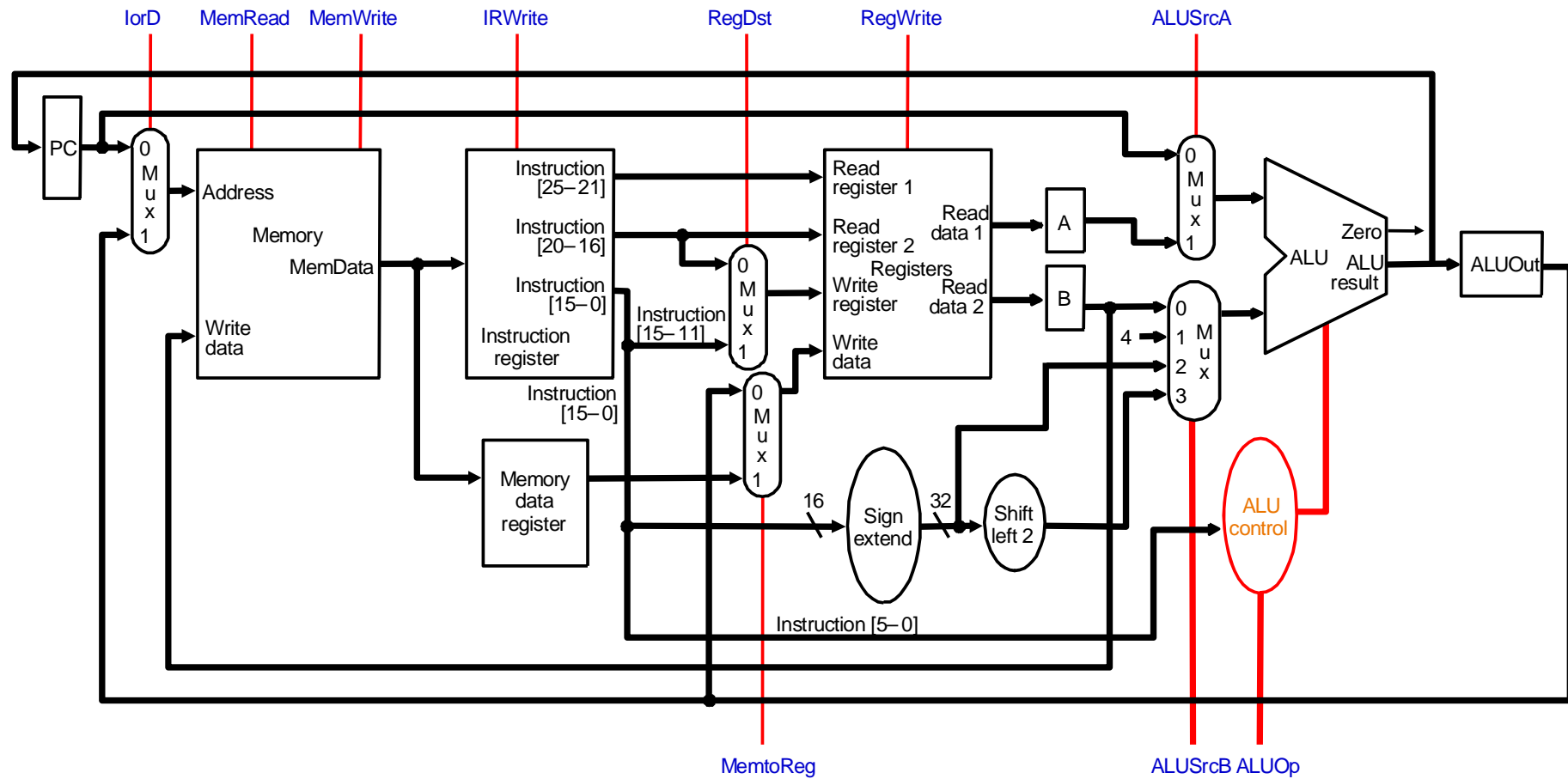
# Control Signals of a Multi-Cycle Datapath



# Complete Control Lines

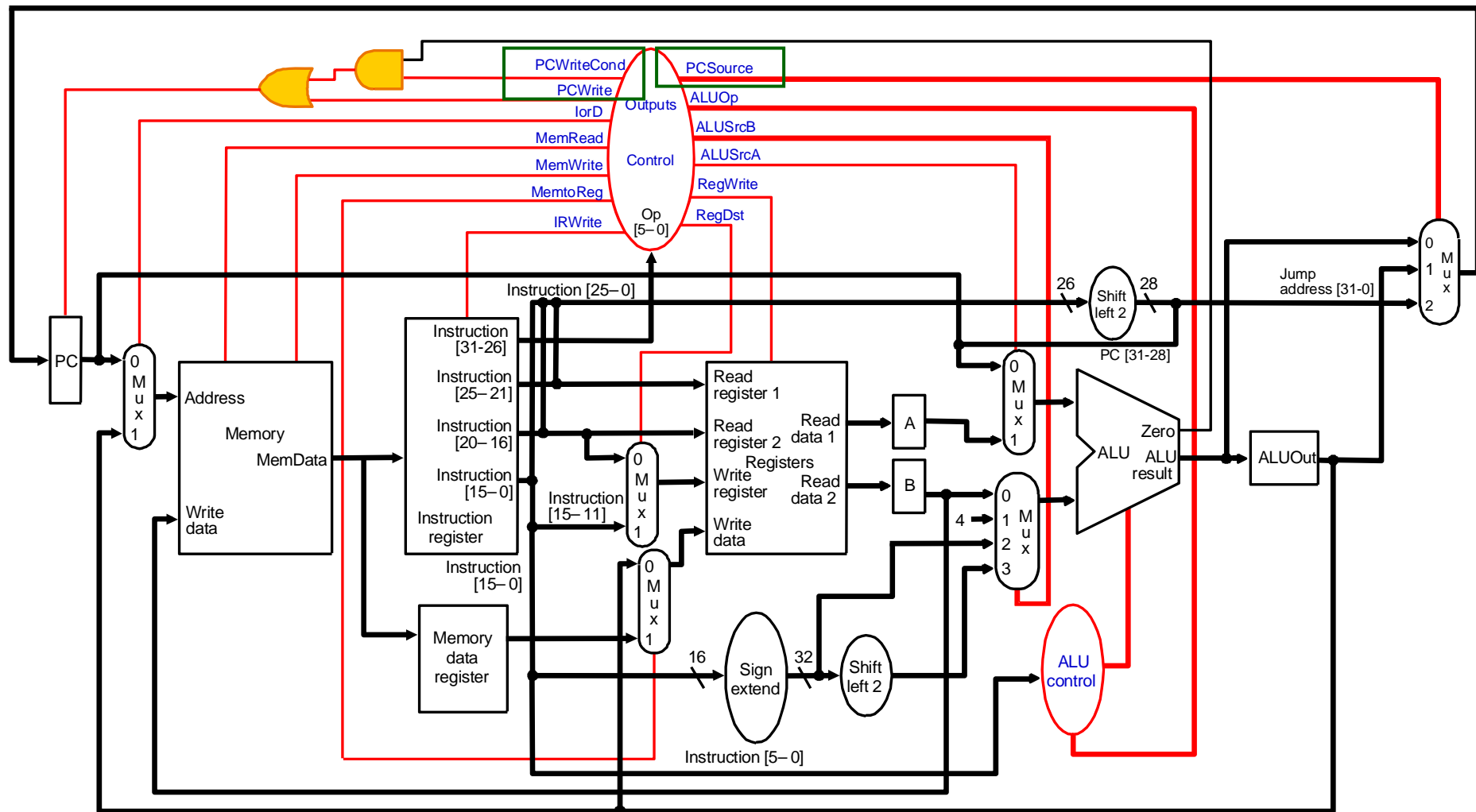

# Five Execution Steps

---

- Instruction Fetch (IF)
- Instruction Decode and Register Fetch (ID)
- Execution, Memory Address Computation, or Branch Completion (EX)
- Memory Access or R-type instruction completion (MEM)
- Write-back step (WB)

# Instruction Fetch (IF)

---

- Use PC to get instruction and put it in the Instruction Register.
- Increment the PC by 4 and put the result back in the PC.
- Can be described succinctly using RTL "Register-Transfer Language"

```
IR = Memory[PC];  
PC = PC + 4;
```


*Can we figure out the values of the control signals?*

- `IR = Memory[PC];` MemRead=1; IRWrite=1; IorD=0;
- `PC = PC + 4;` ALUSrcA=0; ALUSrcB=01; ALUOp=00 (add);  
PCSource=00; PCWrite=1

# Instruction Fetch Control
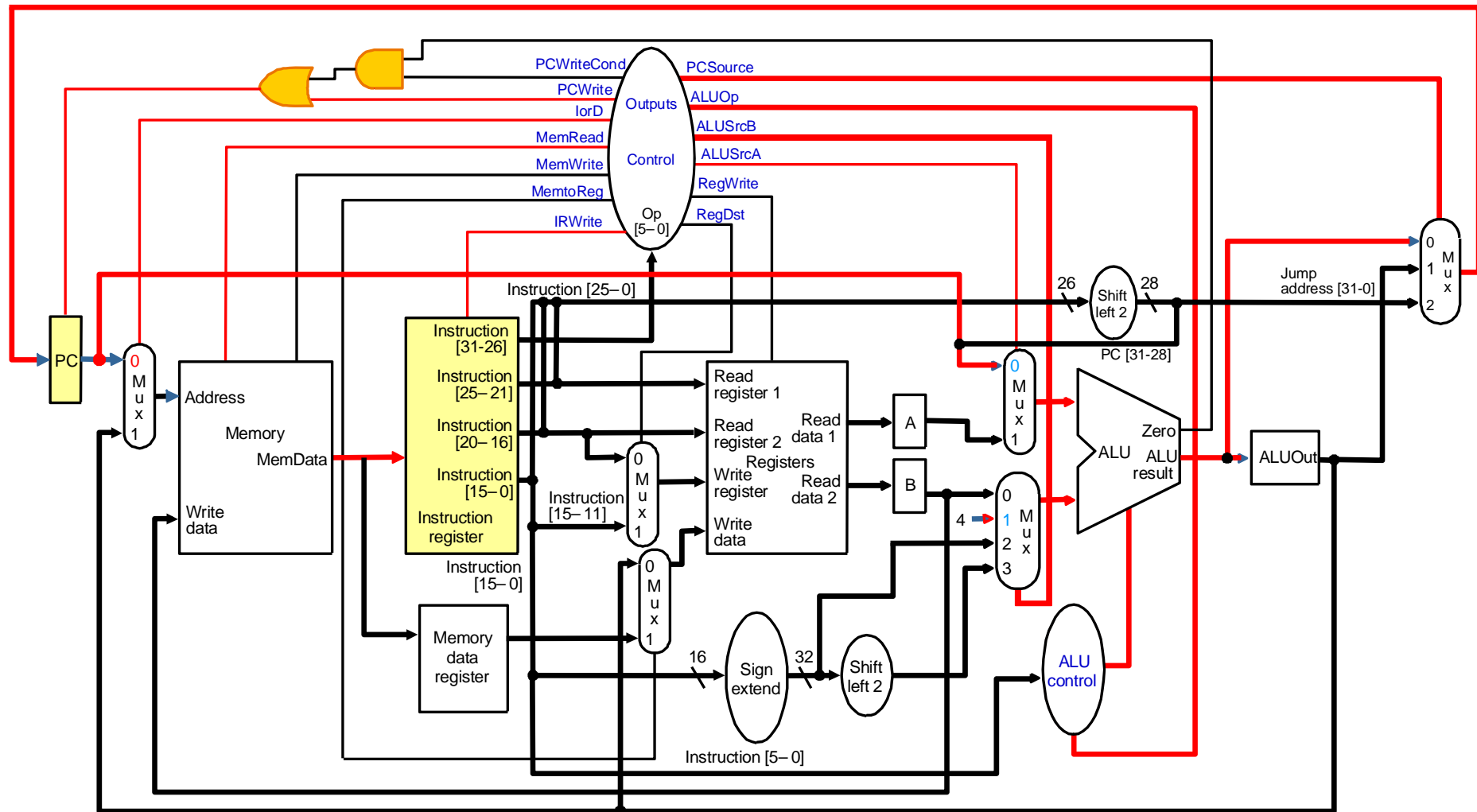
## $IR = \text{Memory}[PC]; PC += 4$

$IR = \text{Memory}[PC];$   $\text{MemRead}=1; \text{IRWrite}=1; \text{IorD}=0;$   
 $PC = PC + 4;$   $\text{ALUSrcA}=0; \text{ALUSrcB}=01; \text{ALUOp}=00 \text{ (add)};$   
 $\text{PCSource}=00; \text{PCWrite}=1$



# Instruction Decode and Register Fetch (ID)

---


- ❑ Still do not have any idea what instruction it is.
- ❑ Read registers rs and rt in case we need them
- ❑ Compute the branch address (used in next cycle in case the instruction is a branch)
- ❑ RTL:

```
A = Reg[IR[25-21]];
B = Reg[IR[20-16]];
ALUOut = PC + (sign-extend(IR[15-0]) << 2);
```

ALUSrcA = 0; ALUSrcB = 11; ALUOp = 00 (add); (for branch target)
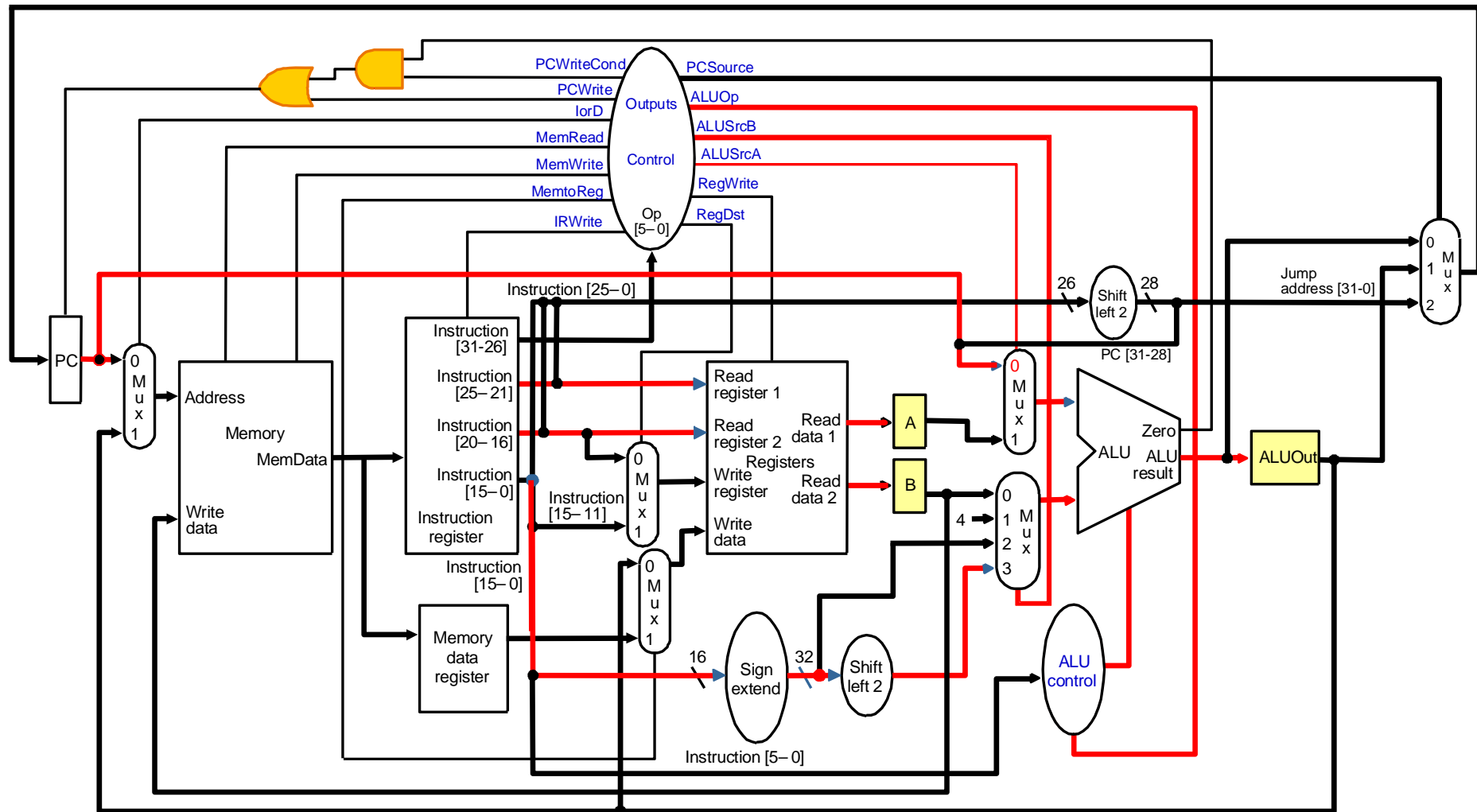
# ID Stage: Assign A and B; Calculate Branch Address

ALUSrcA = 0; ALUSrcB = 11; ALUOp = 00 (add); (for branch target)



# Execute, memory or branch (EX: instruction dependent)

---

- The first cycle, the operation is determined by the instruction class
- ALU is performing one of the following functions, based on instruction type
- **Memory Reference:**

```
ALUOut = A + sign-extend(IR[15:0]);
ALUSrcA=1; ALUSrcB=10; ALUOp=00 (add)
```
- **R-type:**

```
ALUOut = A op B;
ALUSrcA=1; ALUSrcB=00; ALUOp=10 (funct, inst[5:0], decides op)
```
- **Branch:**

```
if (A==B) PC = ALUOut;
PCSource=01; ALUSrcA=1; ALUSrcB=00; ALUOp=01 (sub);
PCWriteCond=1; PCWrite=0;
```
- **Jump:**


```
PC = {PC[31:28] || IR[25:0] << 2'b00};
PCSource=10; PCWrite=1;
```



# Execute: Memory Type
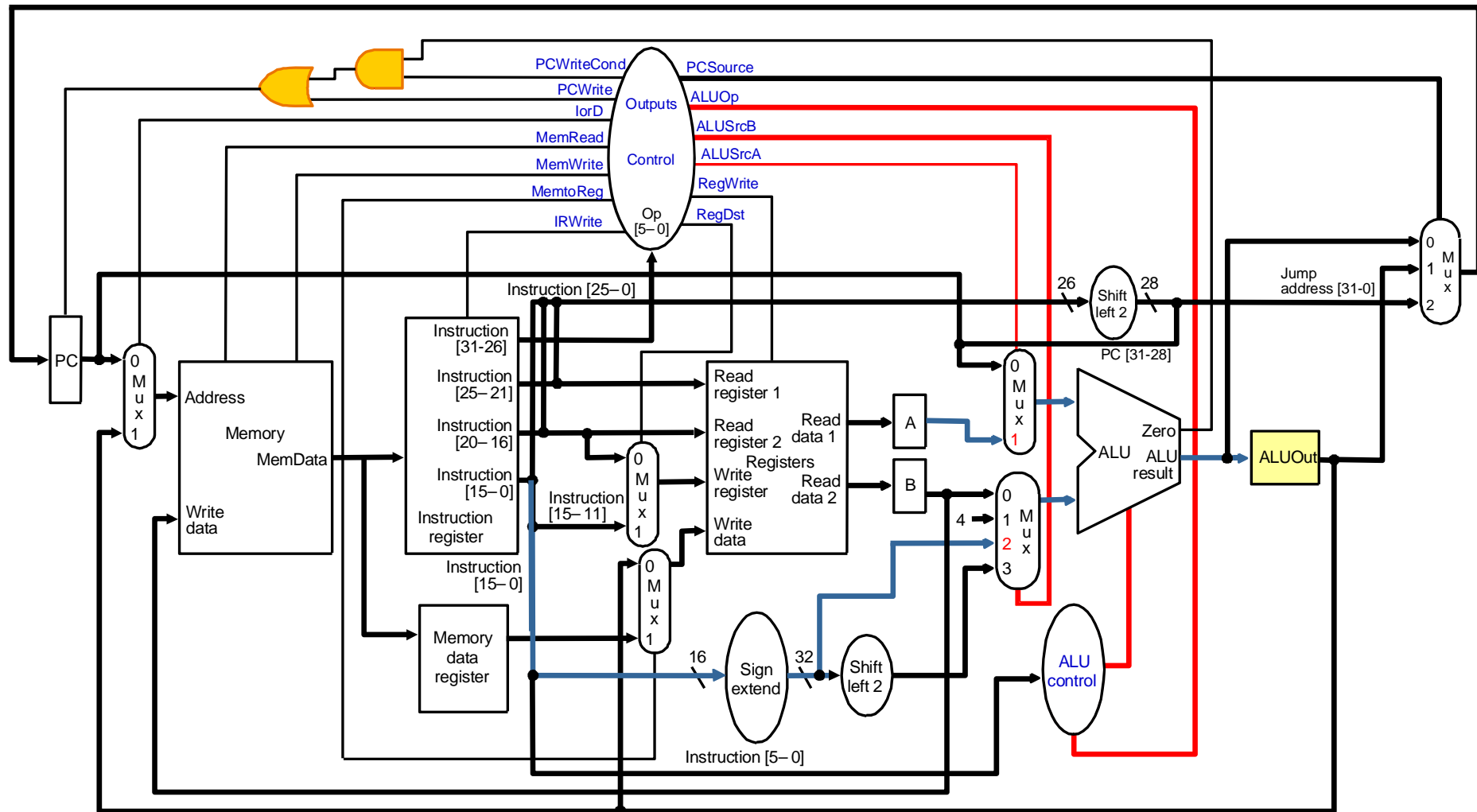
## $ALUOut = A + \text{offset (address)}$


$ALUOut = A + \text{sign-extend}(IR[15-0]);$   
 $ALUSrcA=1; ALUSrcB=10; ALUOp=00 \text{ (add)}$



# Execute: R- Type
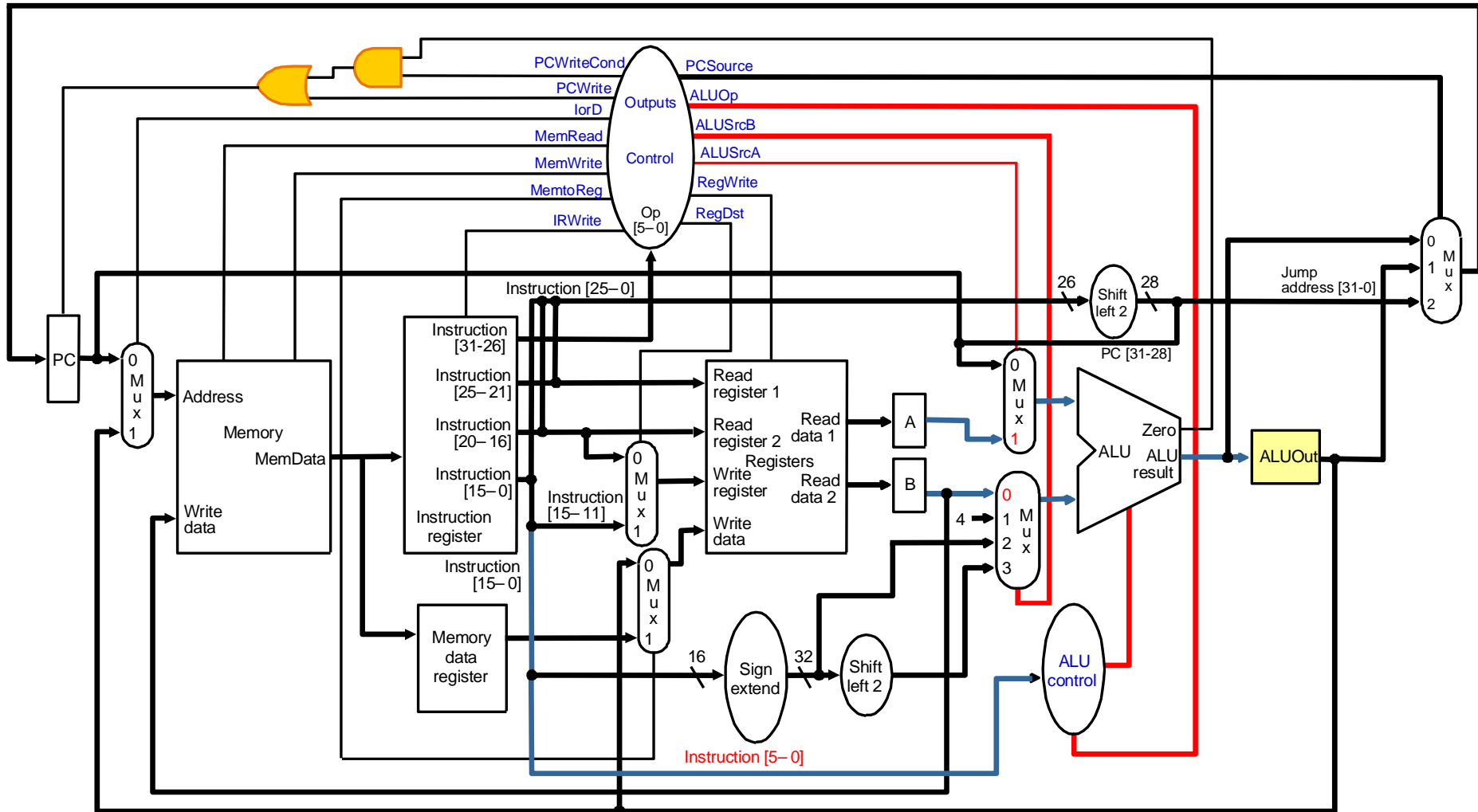
## ALUOut = A op B


ALUOut = A op B;  
 ALUSrcA=1; ALUSrcB=00; ALUOp=10 (funct, inst[5:0], decides op)



# Execute: Branch Type

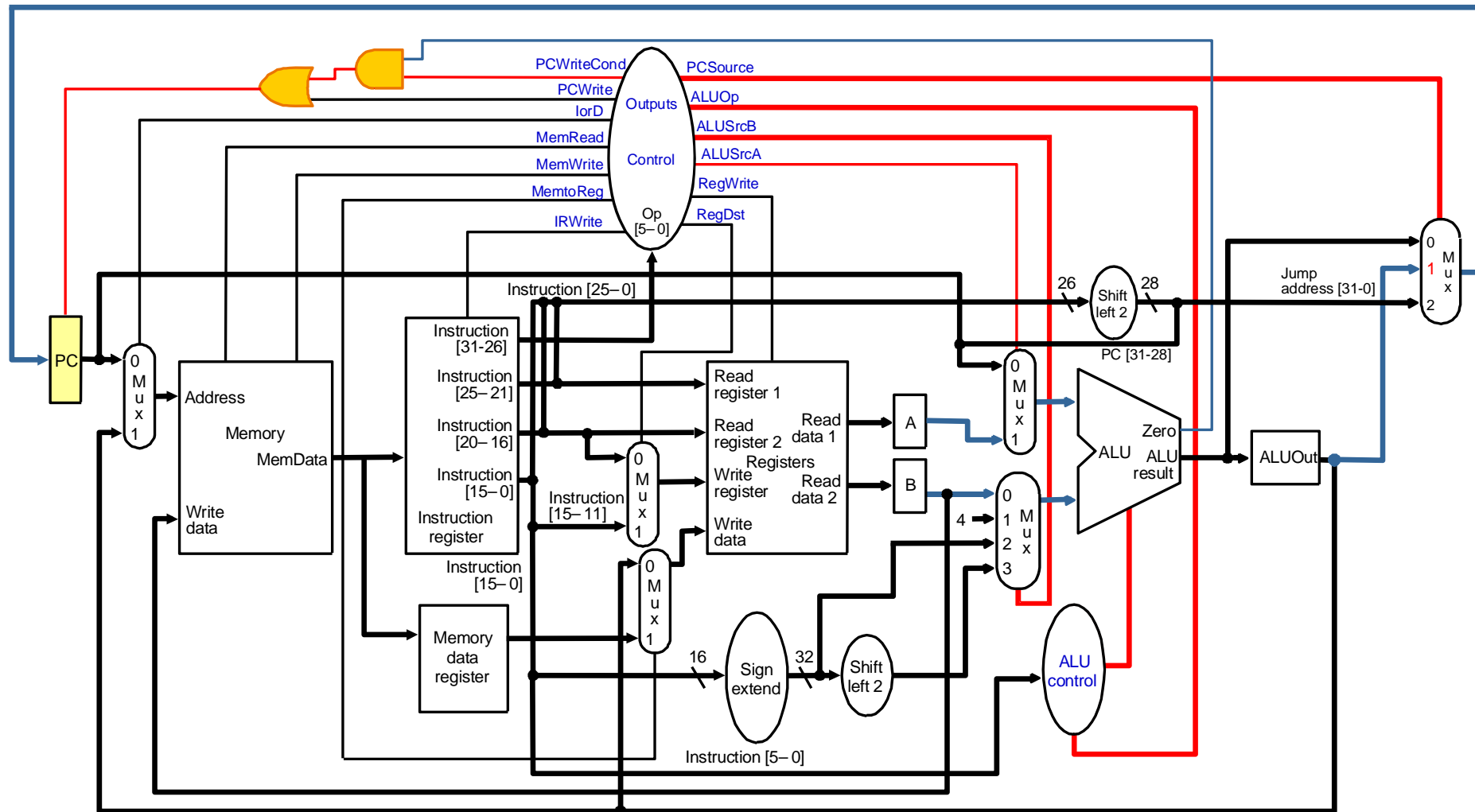
## if (A==B) PC=ALUOut

```
if (A==B) PC = ALUOut;
PCSource=01; ALUSrcA=1; ALUSrcB=00; ALUOp=01 (sub); PCWriteCond=1; PCWrite=0;
```



# Execute: Jump Type (New PC)

```
PC = {PC[31:28] || IR[25:0] << 2'b00};  
PCSource=10; PCWrite=1;
```

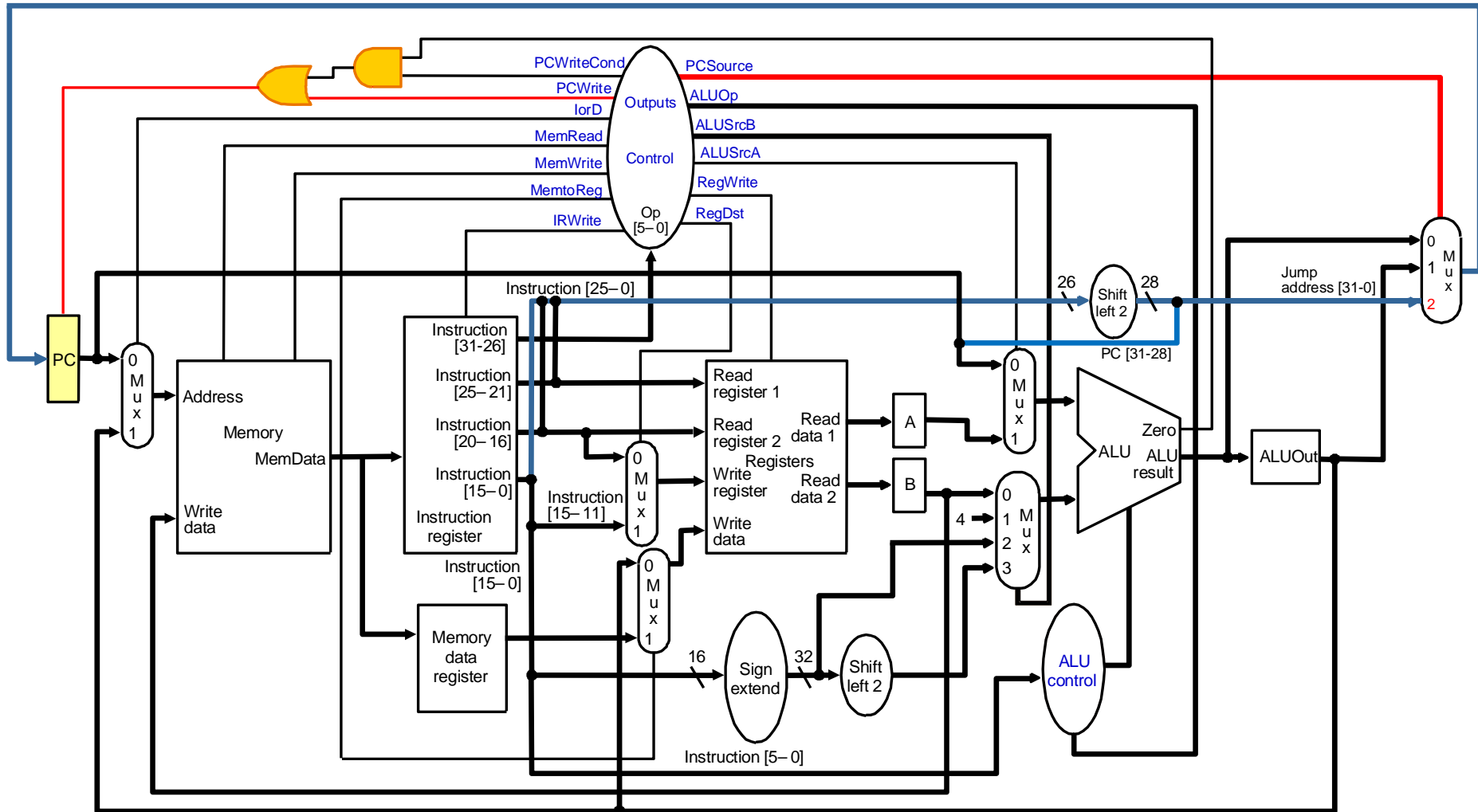

# Memory Access or R-Type

---

- Loads and stores access memory

`MDR = Memory[ALUOut]; lorD=1; MemRead=1;`


or

`Memory[ALUOut] = B; lorD=1; MemWrite=1`


- R-type instructions finish

`Reg[IR[15-11]] = ALUOut; RegDst=1; MemtoReg=0;`  
`RegWrite =1`


# MEM: Load

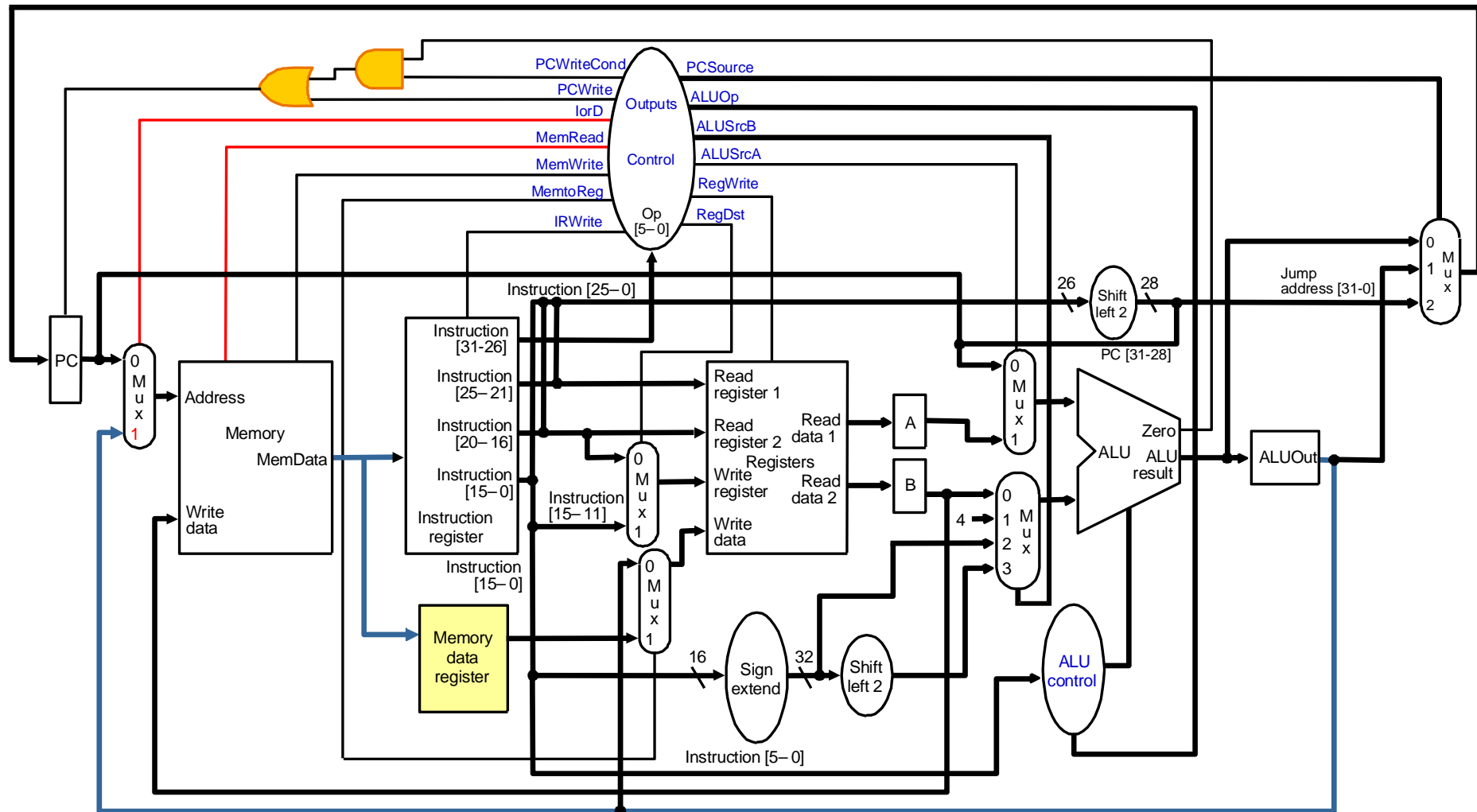

# MEM: Store

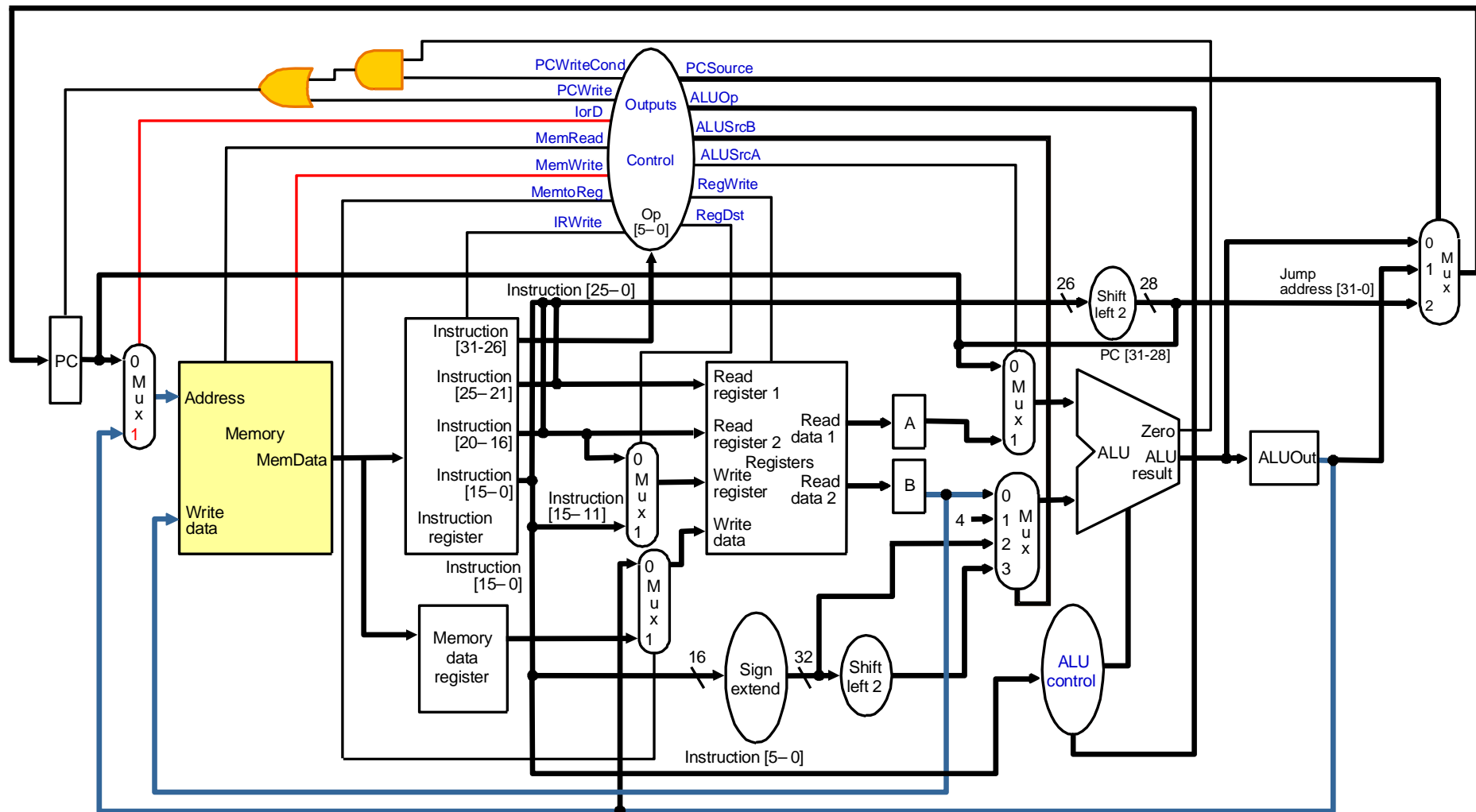

# MEM: R-Type Completion

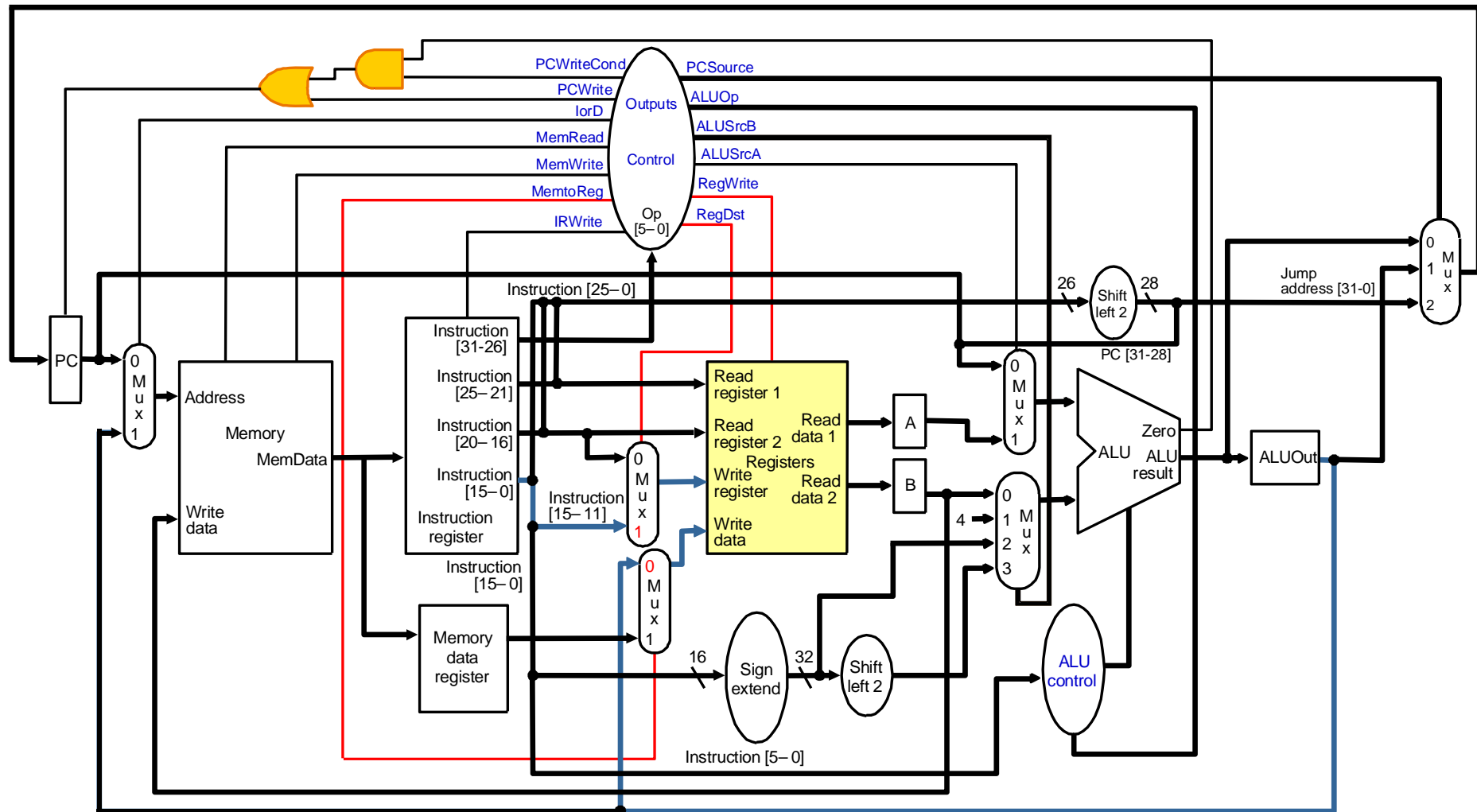




# Write-back for load operation

---

□ `Reg[IR[20-16]] = MDR; MemtoReg=1; RegWrite=1; RegDst=0;`

*What about all the other instructions?*

# WB for Load

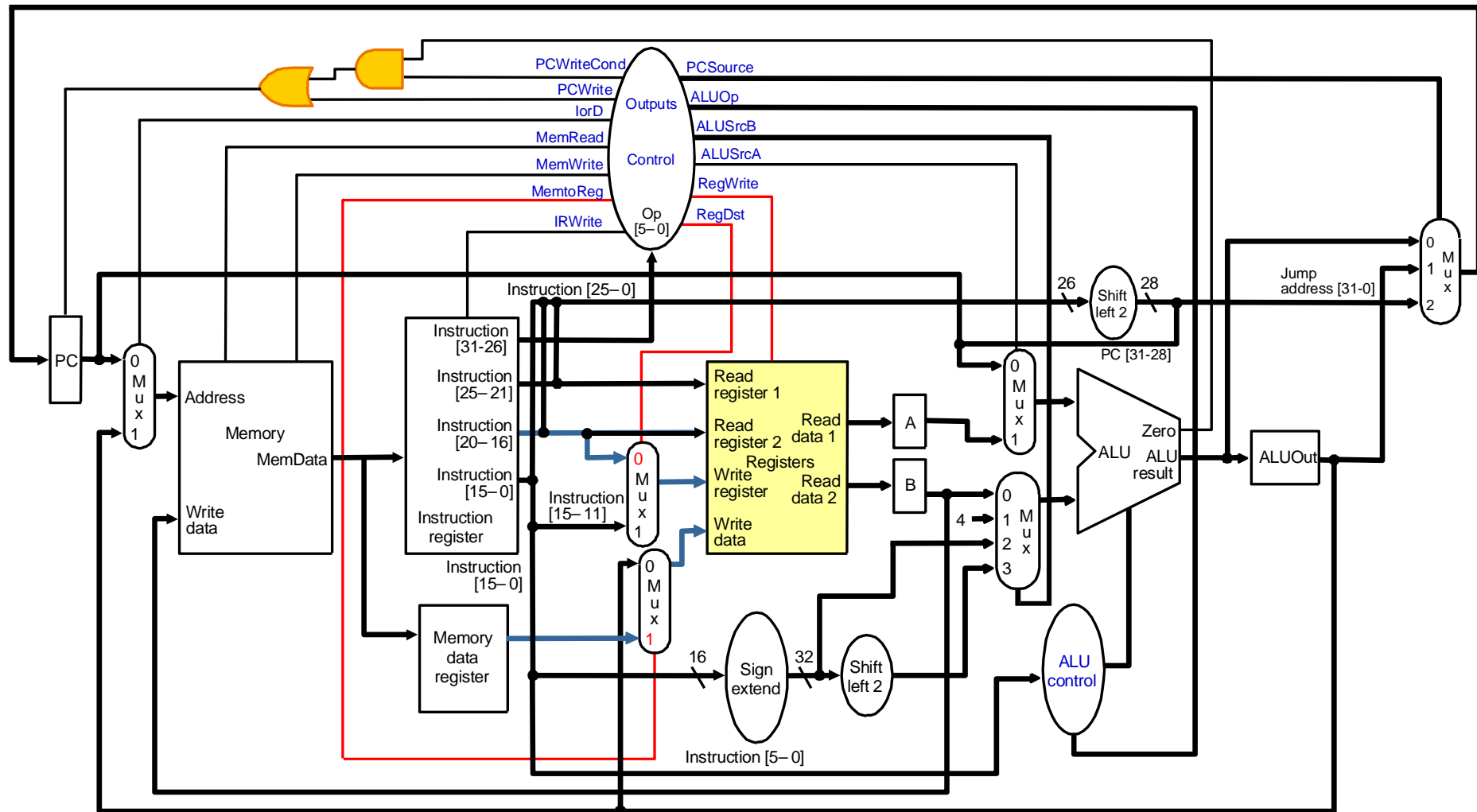

# Summary

---

| Step name   | Action for R-type instructions   | Action for memory-reference instructions  | Action for branches                 | Action for jumps                            |
|---|--|---|-------------------------------------|---|
| Instruction fetch                                       | $IR = \text{Memory}[PC]$<br>$PC = PC + 4$  |   |                                     |   |
| Instruction decode/register fetch                       | $A = \text{Reg}[IR[25-21]]$<br>$B = \text{Reg}[IR[20-16]]$<br>$ALUOut = PC + (\text{sign-extend}(IR[15-0]) \ll 2)$ |   |                                     |   |
| Execution, address computation, branch/ jump completion | $ALUOut = A \text{ op } B$   | $ALUOut = A + \text{sign-extend}(IR[15-0])$                                     | if $(A == B)$ then<br>$PC = ALUOut$ | $PC = PC[31-28] \parallel (IR[25-0] \ll 2)$ |
| Memory access or R-type completion                      | $\text{Reg}[IR[15-11]] = ALUOut$   | Load: $MDR = \text{Memory}[ALUOut]$<br>or<br>Store: $\text{Memory}[ALUOut] = B$ |                                     |   |
| Memory read completion                                  |  | Load: $\text{Reg}[IR[20-16]] = MDR$   |                                     |   |

# Simple Questions

---

- How many cycles will it take to execute this code?

```

        lw $t2, 0($t3)
        lw $t3, 4($t3)
        beq $t2, $t3, Label           #assume not
        add $t5, $t2, $t3
        sw $t5, 8($t3)
Label:    ...
    
```

- What is going on during the 8th cycle of execution?
- In what cycle does the actual addition of \$t2 and \$t3 takes place?



# Implementing the Control

---

- Value of control signals is dependent upon:
  - what instruction is being executed
  - which step is being performed
  
- Use the information we've accumulated to specify a finite state machine
  - specify the finite state machine graphically, or
  - use microprogramming
  
- Implementation can be derived from specification

# Graphical Specification of FSM

